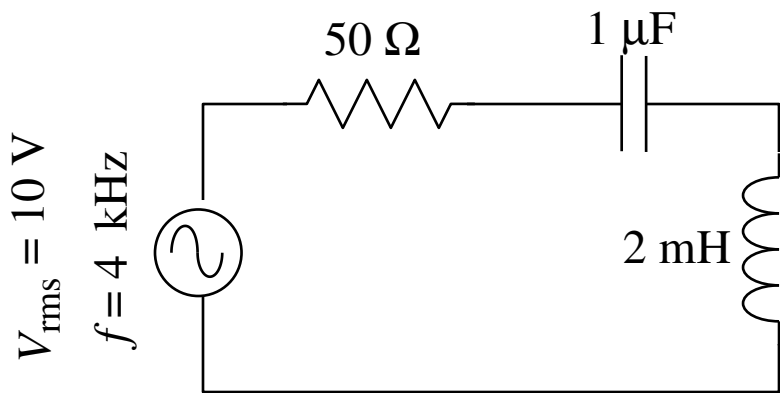


**Quiz 7**

- (A) Calculate the reactance of components:  $C$  and  $L$ . (B) Calculate the total impedance of the circuit.  
(C) Calculate the rms current flowing. (D) Calculate the rms voltage drop across  $R$ .

**Quiz 7**

- (A) Calculate the reactance of components:  $C$  and  $L$ . (B) Calculate the total impedance of the circuit.  
(C) Calculate the rms current flowing. (D) Calculate the rms voltage drop across  $R$ .

