

8. What is the maximum current delivered to a circuit containing a  $2.20\text{-}\mu\text{F}$  capacitor when it is connected across (a) a North American outlet having  $\Delta V_{\text{rms}} = 120\text{ V}$  and  $f = 60.0\text{ Hz}$  and (b) a European outlet having  $\Delta V_{\text{rms}} = 240\text{ V}$  and  $f = 50.0\text{ Hz}$ ?
15. An inductor has a  $54.0\text{-}\Omega$  reactance at  $60.0\text{ Hz}$ . What will be the *maximum* current if this inductor is connected to a  $50.0\text{-Hz}$  source that produces a  $100\text{-V}$  rms voltage?
57. As a way of determining the inductance of a coil used in a research project, a student first connects the coil to a  $12.0\text{-V}$  battery and measures a current of  $0.630\text{ A}$ . The student then connects the coil to a  $24.0\text{-V}$  (rms),  $60.0\text{-Hz}$  generator and measures an rms current of  $0.570\text{ A}$ . What is the inductance?
- 31.14** • You have a  $200\text{-}\Omega$  resistor, a  $0.400\text{-H}$  inductor, and a  $6.00\text{-}\mu\text{F}$  capacitor. Suppose you take the resistor and inductor and make a series circuit with a voltage source that has voltage amplitude  $30.0\text{ V}$  and an angular frequency of  $250\text{ rad/s}$ . (a) What is the impedance of the circuit? (b) What is the current amplitude? (c) What are the voltage amplitudes across the resistor and across the inductor? (d) What is the phase angle  $\phi$  of the source voltage with respect to the current? Does the source voltage lag or lead the current? (e) Construct the phasor diagram.

**31.40** •• Five infinite-impedance voltmeters, calibrated to read rms values, are connected as shown in **Fig. P31.40**. Let  $R = 200\text{ }\Omega$ ,  $L = 0.400\text{ H}$ ,  $C = 6.00\text{ }\mu\text{F}$ , and  $V = 30.0\text{ V}$ . What is the reading of each voltmeter if (a)  $\omega = 200\text{ rad/s}$  and (b)  $\omega = 1000\text{ rad/s}$ ?

Figure **P31.40**

