

## Kirchhoff's Laws

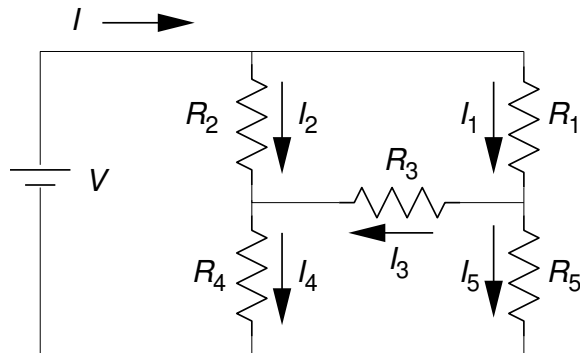


Figure 1: The above circuit was devised by Charles Wheatstone in 1843, and hence is often called a Wheatstone bridge. Generally it is set up so that  $V$ ,  $R_2$ – $R_5$  are known values, and  $R_1$  is varied until  $I_3$  is zero.


## 1 Discussion

Gustav Kirchhoff (1824–1887) discovered two laws which describe the current flow in dc circuits:

1. The sum of the currents flowing away from any point in a circuit is equal to the sum of the currents flowing toward that point. For example, in the above circuit we must have:

$$I_1 = I_3 + I_5$$

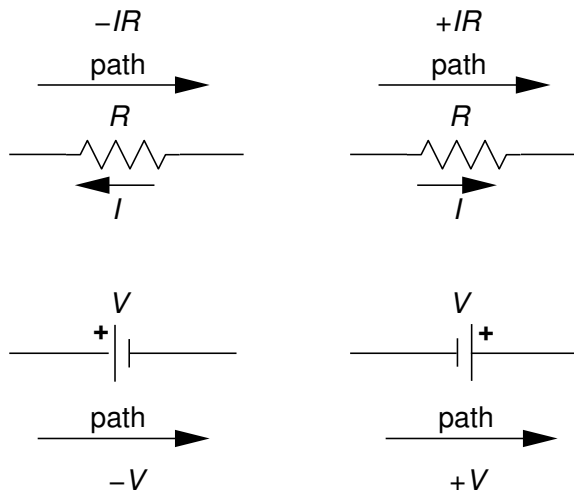2. In traversing any closed path in a circuit the sum of the emfs (e.g., battery voltages) is equal to the sum of the  $IR$  voltage drops from resistors. The sign of the emfs and  $IR$  drops is determined by the traversal direction, battery polarity, and assumed direction of  $I$  as follows:



For example, in the above circuit one path gives the equation:

$$V = I_2 R_2 - I_3 R_3 + I_5 R_5$$

## 2 Homework

If we consider  $V$  and  $R_1-R_5$  as fixed there are six unknowns:  $I, I_1-I_5$ . Write down six independent linear equations relating these unknowns, and solve the resulting system of linear equations with `Solve`. Use *Mathematica* to find an expression for  $I_3$ :

$$\text{Out}[4]= \frac{r_1 r_4 - r_2 r_5}{(r_3 r_4 + r_2 (r_3 + r_4)) r_5 + r_1 (r_4 (r_3 + r_5) + r_2 (r_3 + r_4 + r_5))}$$

Show that  $I_3 = 0$  only if

$$\frac{R_1}{R_5} = \frac{R_2}{R_4}$$

(Since *Mathematica* likes to reserve capital letters for its own use, I used `r1`, `r2`, ... for  $R_1, R_2, \dots$ )

Turn in a printout showing each step as *Mathematica* solves the problem.