

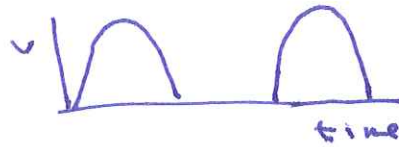



Rectification

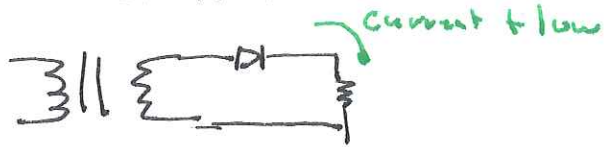

"half wave"

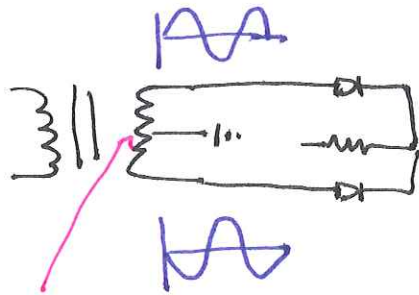


"center tapped"

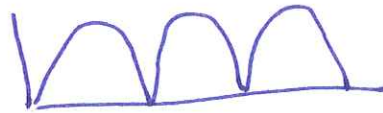

"full wave"

$$f = 120 \text{ Hz}$$


Full wave bridge with 2 diode drop.

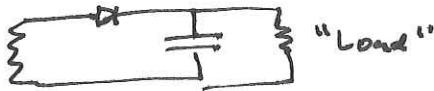


"Load"

$R_{TH}?$
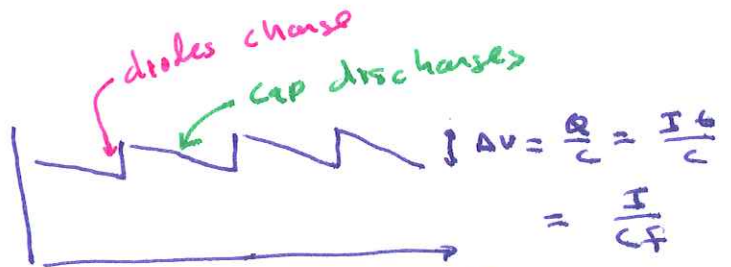
$$V_{DC} = V_0 - \frac{1}{2} \frac{I_T}{C}$$



What is V_{rms} of a sawtooth?

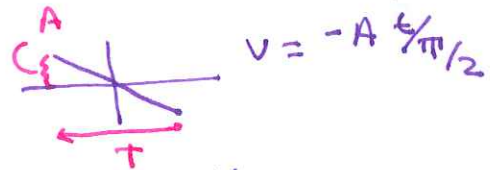

$$\langle V^2 \rangle = \frac{1}{T} \int_{-T/2}^{T/2} (-A t / (\pi/2))^2 dt = \frac{4A^2}{\pi^3} \int_0^{T/2} t^2 dt$$

$$= \frac{A^2}{3} \rightarrow V_{rms} = \frac{A}{\sqrt{3}}$$

$$V_{rms} = \frac{1}{\sqrt{3}} \frac{I_T \pi/2}{C}$$

3 terminal regulator

