

BJT Golden Rules

1) $I_E = I_C$ (ok: $I_E = I_C + I_B$ but generally $I_C \gg I_B$
 in fact (see below) $I_C = \beta I_B \Rightarrow I_E = (\beta + 1) I_B$)

$V_B = V_E + 0.6$ (ok: the 'turn-on' voltage of a forward biased PN junction varies with temperature; larger I_B does mean larger V_{BE} but during normal operation V_{BE} typically varies only $\pm \frac{1}{40} V$ - small change)


Common Emitter Amp



$$\Delta I_E = \frac{\Delta V_B}{R_E}$$

$$\Delta V_{out} = -R_C \Delta I_C = -\frac{R_C}{R_E} \Delta V_B$$

Emitter Follower

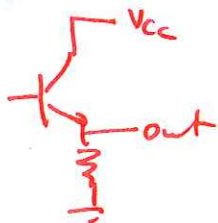


$$\Delta V_{out} = \Delta V_B$$

2) $I_C = \beta I_B$ (but: range of β allowed by specs large.
 β not constant - varies with I_B)

Avoid circuits that depend on a particular value of β - they may not work with replacement transistor.

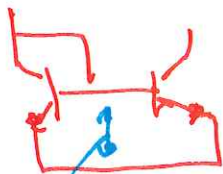
3) I_B, I_C in fact functions of V_{BE} - match V_{BE} match results. (For a "matched pair")



same V_{BE} - same currents thru device.

FETs vs Bipolar Junction Transistors


2 basic types n-channel & p-channel

 

The controlling terminal is a PN junction: diode

Back Biased Diode

therefore intrinsic high input impedance

 

As electrons/holes diffuse & combine in "foreign" soil charge layers build up near junction. Eventually the resulting \bar{E} is large enough to stop further diffusion (dynamic equilibrium)

The resulting V barrier literally keeps a lid on diffusion - chance that barrier & expo more current flows:

$$I \approx I_0 e^{\frac{eV}{kT}} \Rightarrow I \approx I_0 e^{\frac{AV}{V_T}} \quad \left(V_T = \frac{kT}{e} \approx \frac{1}{40} V \right)$$

$$\frac{dI}{dV} \equiv \frac{1}{r} = \frac{1}{V_T} I_0 e^{V/V_T} = \frac{I}{V_T} \Rightarrow r = \frac{V_T}{I} = \frac{1000 V_T}{I(\text{mA})}$$

ac resistance

$$= \frac{25 \Omega}{I(\text{mA})}$$

"engineers' e_8 "

2 basic types NPN & PNP




The controlling terminal is a PN junction: diode

Forward Biased Diode

therefore intrinsic low input impedance

 The characteristic curves are labelled with gate voltage




plateaus are spaced quadratically $I_D \propto (V_{GS} - V_T)^2$

AC behavior (Taylor Expansion)

$$I_D(V_{DS}, V_{GS})$$


$$dI_D = \underbrace{\frac{\partial I_D}{\partial V_{DS}}}_{y_{os}} dV_{DS} + \underbrace{\frac{\partial I_D}{\partial V_{GS}}}_{y_{fs} = g} dV_{GS}$$

admittance

 

"saturated" = active region where I_D plateaus

 The characteristic curves are labelled with base current




plateaus are spaced linearly $I_C \propto I_B$

$$I_C(V_{CE}, I_B)$$

$$dI_C = \underbrace{\frac{\partial I_C}{\partial V_{CE}}}_{h_{oe}} dV_{CE} + \underbrace{\frac{\partial I_C}{\partial I_B}}_{h_{fe} = \beta} dI_B$$

hybrid

 

"saturated" = region where V_{CE} is small - same approx location as "linear region" in FET

The gate draws essentially zero current: $I = I_0 (e^{V_{BE}/V_T} - 1)$

so DC corresponds to h_{FE} ; AC corresponds to capacitor.

The base must draw current to be in active region & hence $\approx kT/q$ DC

$$[r = \frac{25\Omega}{I_B(\text{mA})}] \text{ AC}$$

there are "stray capacitance" to both emitter & collector but we will largely ignore these.


$$dV_{BE} = \frac{\partial V_{BE}}{\partial V_{CE}} dV_{CE} + \frac{\partial V_{BE}}{\partial I_B} dI_B$$

$h_{re} \approx 10^{-4}$
often ignored

$$h_{ie} \text{ (unit } \Omega \approx \frac{25\Omega}{I_B(\text{mA})})$$




 REMARK: Ht thinks if input base resist as actually connected to emitter:



r_e is smaller than h_{ie} (due to $I_C \approx I_B$ flow thru it) but its voltage effect on h_{be} is multiplied by $(\beta+1)$ so net result is exactly as h_{ie} . Thinking about it as if in emitter allows it to be combined with actual emitter resistors to make nicer formulas

Do Not Build this Circuit! (theory only)

 

since $V_{Base} = 0.6V$ (fixed)

$$\Delta I_B = \frac{\Delta V_{in}}{R_G}$$

$$\Delta I_C = \beta \Delta I_B$$

$$\Delta V_{out} = -R_C \Delta I_C$$

$$= -\frac{R_C}{R_G} \beta \Delta V_{in}$$

→ voltage gain A_v

$$A_v = -\frac{R_C}{R_G} \beta$$

There are several things wrong with this analysis

Note $A_v = \infty$ is implied if $R_G \rightarrow 0$

you will show eventually max A_v of this

circuit is $20 \times V_{cc}$

[of course you know going for max gain is a
mistake — throw away that gain with negative
feedback to improve circuit performance]