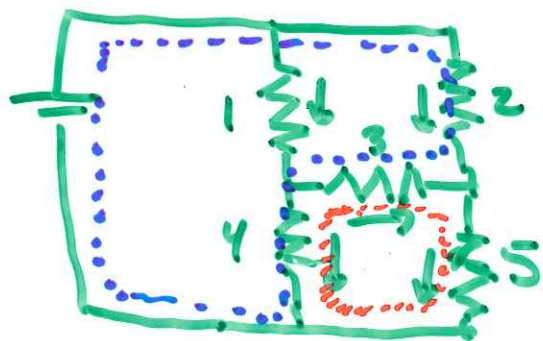


In circuits with single frequency sinusoidal drives we can treat  $L \neq C$  as if  $R$  but with complex "resistance" = impedance  $i\omega L \neq \frac{1}{i\omega C}$

IF drive is not sinusoidal use Superposition & Fourier

Kirchhoff: ①  $\sum V = 0$  ②  $\sum I = 0$




$$V - I_2 R_2 + I_3 R_3 - I_4 R_4 = 0$$

$$-I_5 R_5 + I_4 R_4 - I_3 R_3 = 0$$

$$I_1 - I_3 - I_4 = 0$$

$$I_2 + I_3 - I_5 = 0$$

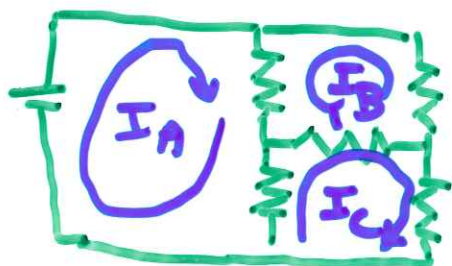Mesh: imagine continuous loop currents that superposition to form actual current




$$"I_1" = I_A - I_B$$

$$"I_3" = I_C - I_B$$






$$"I_2" = I_B$$

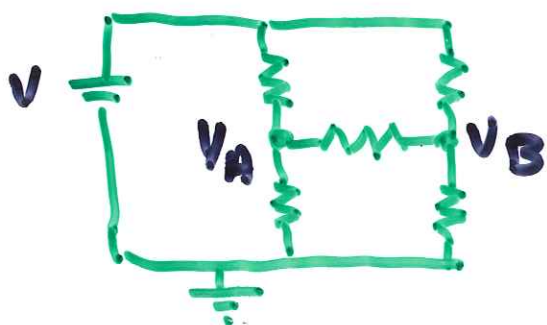
Node: assign a ground ( $V=0$ ) & unknown voltages to every junction; write  $\sum I = 0$



$$\frac{(V - V_A)}{R_1} + \frac{(V_B - V_A)}{R_3} + \frac{(0 - V_A)}{R_2} = 0$$
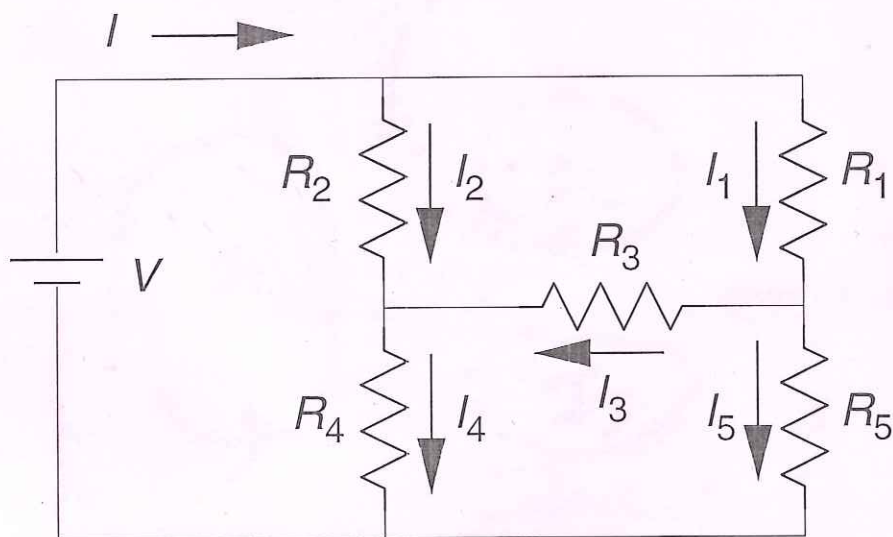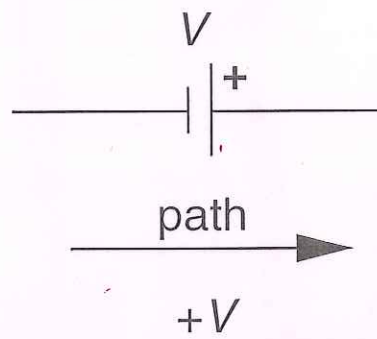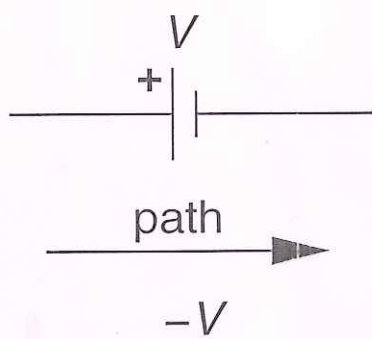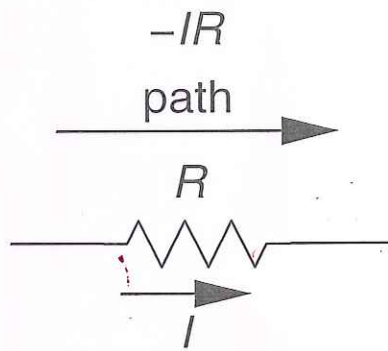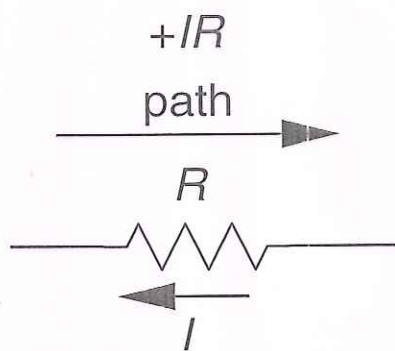
$$\frac{(V - V_B)}{R_4} + \frac{(V_A - V_B)}{R_3} + \frac{(0 - V_B)}{R_5} = 0$$





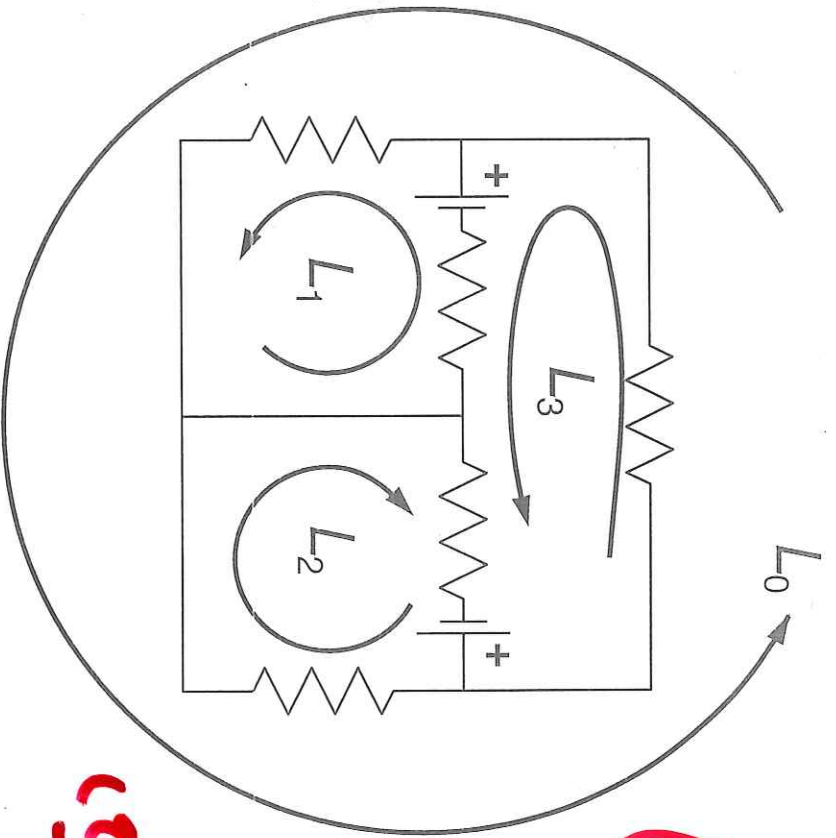

**K**


**E**

**FET**

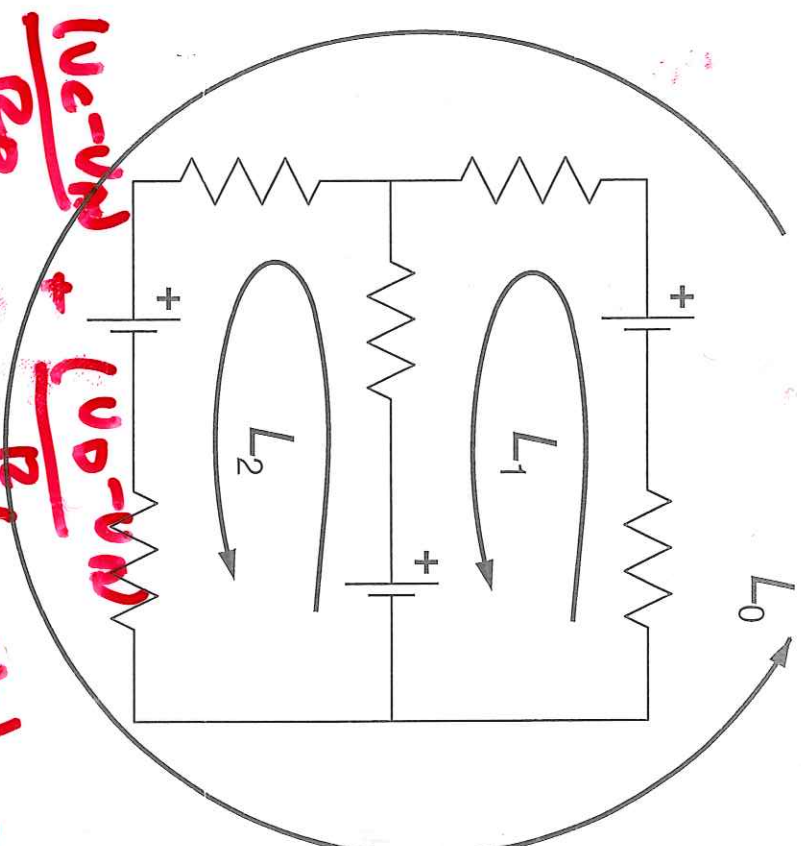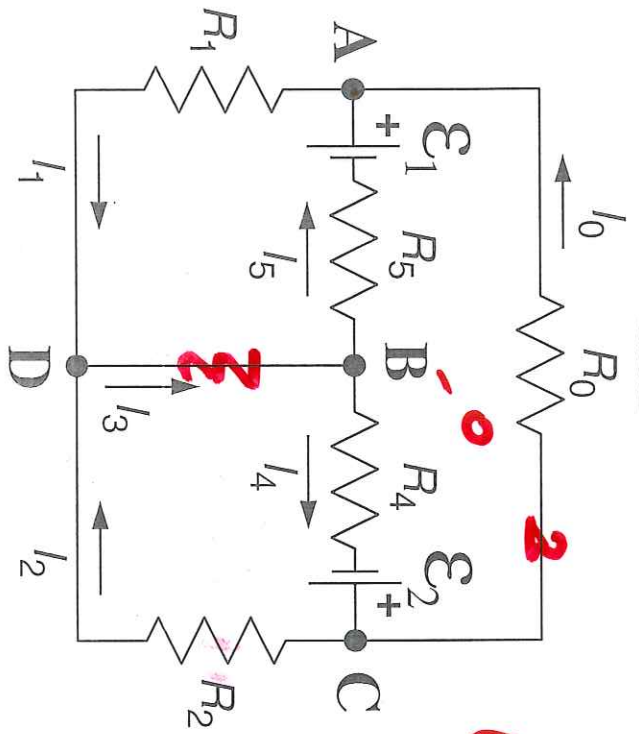

$$\frac{(\mathcal{E}_1 - V_A)}{R_5} + \frac{(V_C - V_A)}{R_0} + \frac{(V_D - V_A)}{R_1}$$


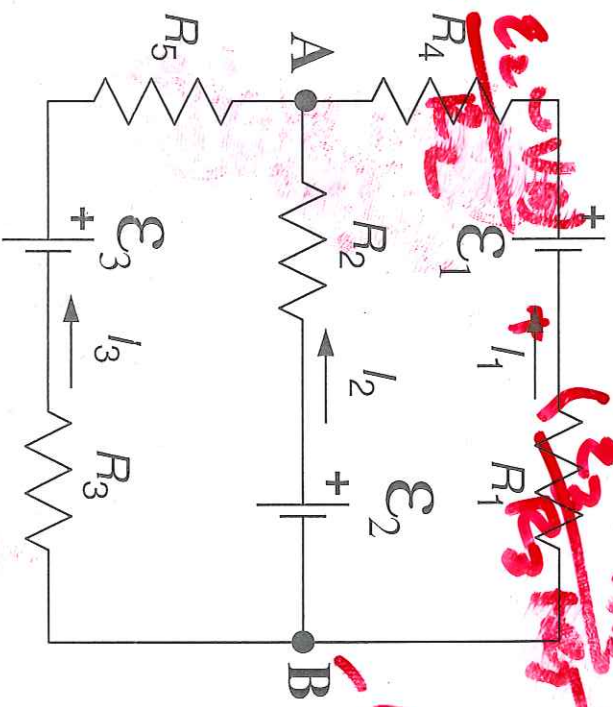
$$+ \frac{(\mathcal{E}_2 - V_A)}{R_4} + \frac{(\mathcal{E}_3 - V_A)}{R_3}$$



$$\frac{(\mathcal{E}_3 - V_A)}{R_3} + \frac{(\mathcal{E}_2 - V_A)}{R_4}$$


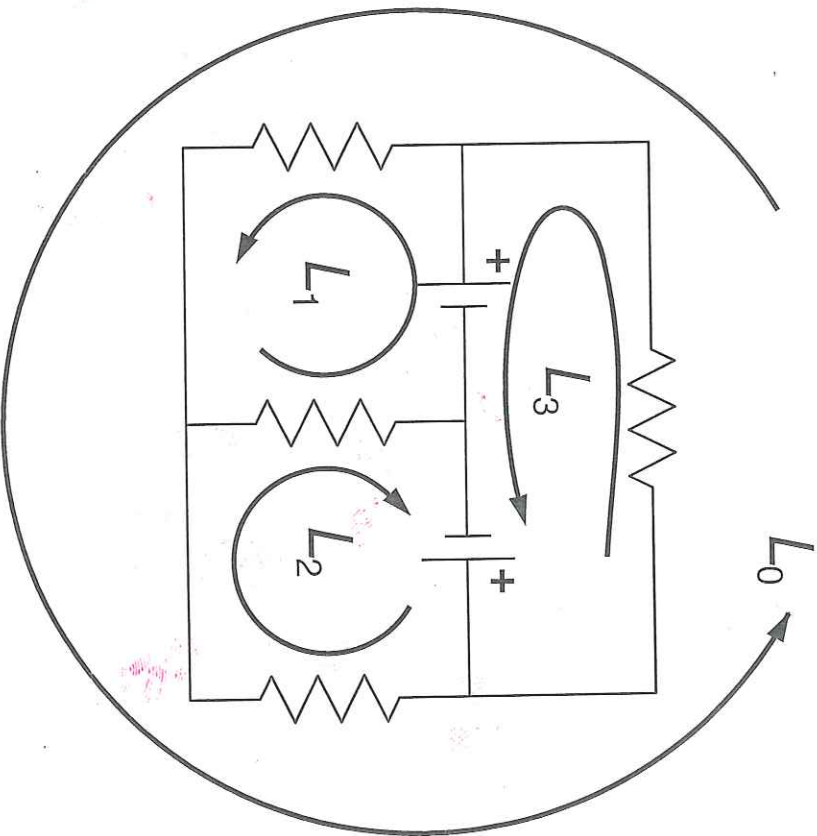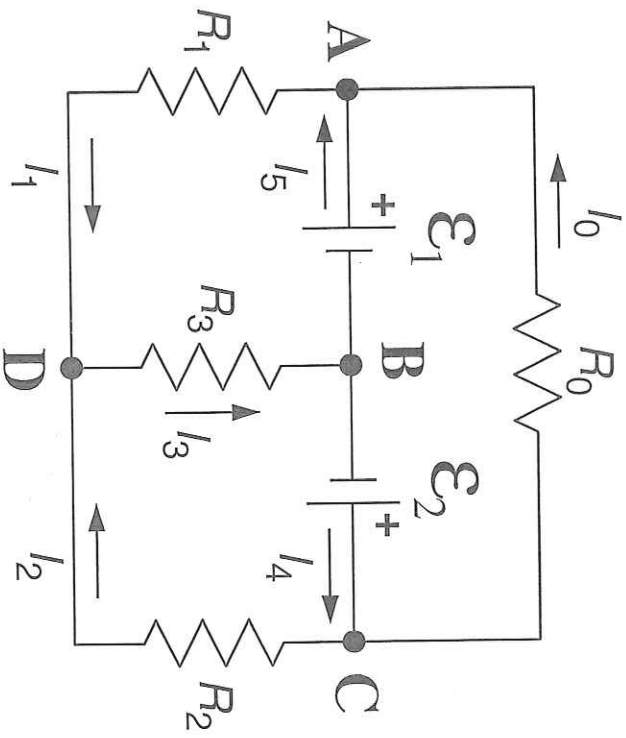
$$\left(\frac{\mathcal{E}_1 - V_B}{R_1}\right) + \left(\frac{\mathcal{E}_2 - V_B}{R_2}\right) + \frac{(0 - V_B)}{R_3} = 0$$



# Power

$$P = VI$$

$$\bar{P} = \frac{VI}{R I_0 \cos(\omega t)} V_0 \cos(\omega t + \phi)$$

$$\cos(\omega t + \phi) = \cos(\omega t) \cos \phi - \sin(\omega t) \sin \phi$$

$$\bar{P} = V_0 I_0 \left( \underbrace{\cos^2(\omega t)}_{\frac{1}{2}} \cos \phi - \underbrace{\sin(\omega t) \cos(\omega t)}_0 \sin \phi \right)$$

$$= \frac{1}{2} V_0 I_0 \cos \phi$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$= V_{rms} I_{rms} \cos \phi$$

power factor



$$\phi = -90^\circ \quad I_{rms}$$



$$\phi = 90^\circ$$


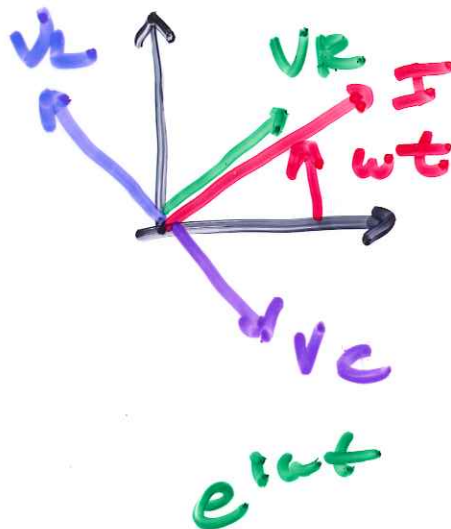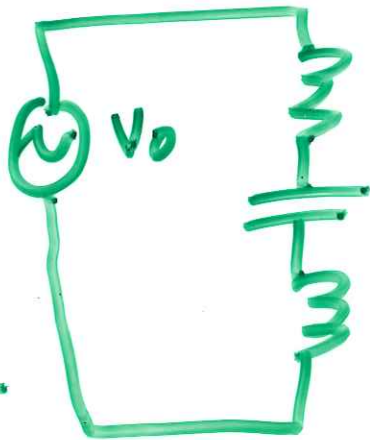
# Resonance

$$Z = i\omega L + \frac{1}{i\omega C} + R$$

$$= i\left(\omega L - \frac{1}{\omega C}\right) + R$$



$$V = V_0 e^{i\omega t}$$


$$I = I_0 e^{i\omega t}$$

$$V = I Z \rightarrow V_0 = Z I_0$$

$$I_0 = \frac{V_0}{Z}$$

$$|I| = \frac{|V_0|}{|Z|}$$

$$= \frac{|V_0|}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

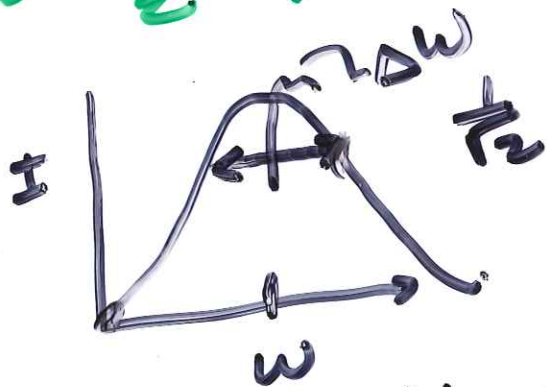

full width  $\Delta \omega$  "1/2 max"

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$f(x_0 + \Delta x) = f(x_0) + f'(x_0) \Delta x + \dots$$

$$\left(\omega L - \frac{1}{\omega C}\right) \Big|_{\omega_0 + \Delta \omega} = R$$


$$0 + \left(L + \frac{1}{\omega^2 C}\right) \Big|_{\omega_0} \Delta \omega = R$$

$$\Delta \omega = \frac{R}{2L}$$

$$2\Delta \omega = \frac{R}{L}$$

$$Q = \frac{\omega_0}{2\Delta\omega} = \frac{\omega_0}{R/L} \Rightarrow \frac{\omega_0 L}{R} = \frac{1}{R\omega_0 C}$$


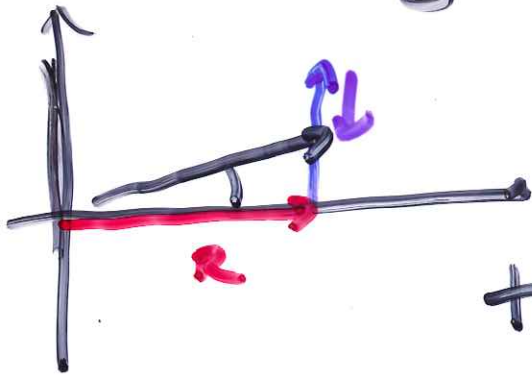
$$Z = R + i(\omega L - \frac{1}{\omega C})$$



$$\tan\phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$\omega \rightarrow 0 \quad \phi = -90^\circ \quad \leftarrow \quad \phi = 0$   
 $\omega \rightarrow \infty \quad \phi = 90^\circ$

Thevenin / Norton


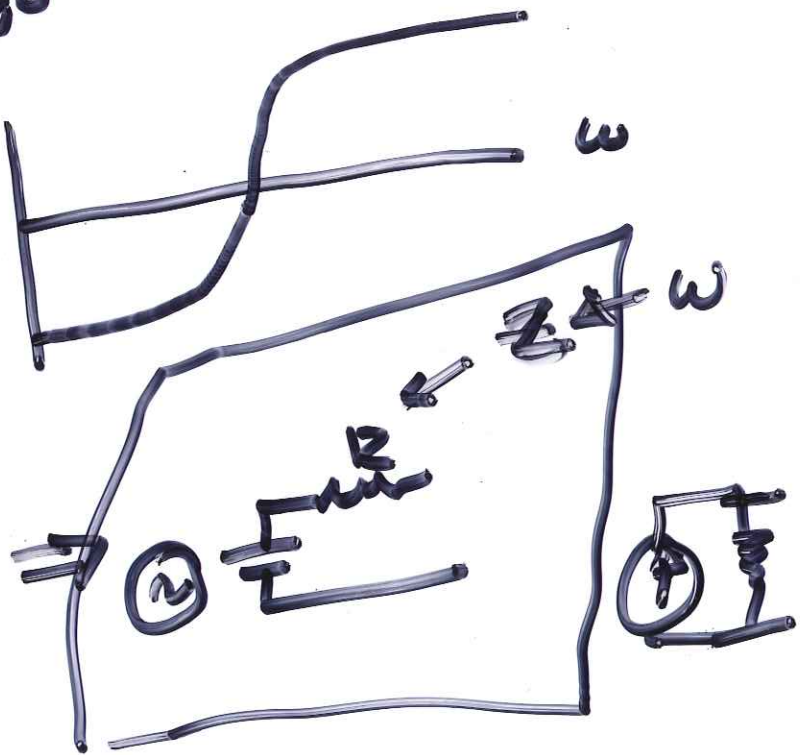
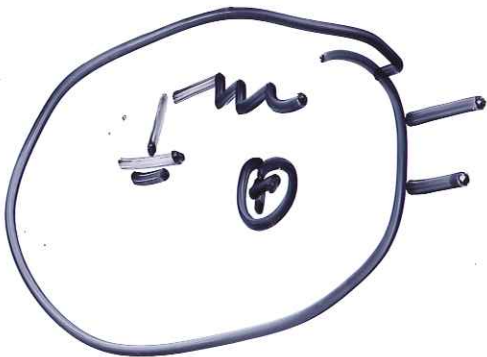


output impedance  
input impedance





Amp

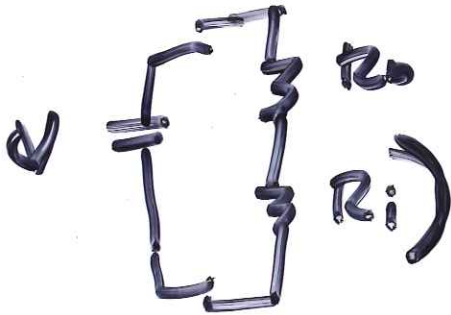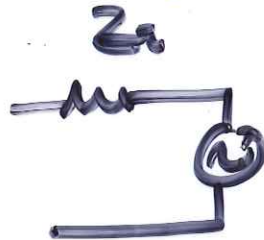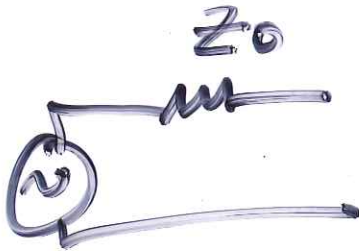

$$I = \frac{V}{R_0 + R_i}$$

$$\frac{V^2}{(R_0 + R_i)^2} R_i \quad \times$$

$$\frac{V^2}{R_0} \left( \frac{R_i/R_0}{1 + (R_i/R_0)} \right)^2$$

$$R_i \rightarrow 0$$

$$R_i \rightarrow \infty$$

$$\frac{x}{(1+x)^2}$$

$$\frac{1}{(1+x)^2} = 2 \frac{x}{(1+x)^3}$$



$$\frac{1+x-2x}{(1+x)^3} = \frac{1-x}{(1+x)^3} = 0$$

$$x=1 \rightarrow R_i = R_0$$

$$Z_i^* = Z_0$$



$$\overline{\operatorname{Re}(V) \operatorname{Re}(I)} = \frac{1}{2} \operatorname{Re} V^* I$$

Im

$$f = f_0 e^{i\omega t}$$

$$g = g_0 e^{i\omega t}$$

$$\operatorname{Re}(f) \operatorname{Re}(g)$$

$$f_0 = a + ib \quad g_0 = c + id$$

$$(a \cos(\omega t) - b \sin(\omega t)) (c \cos(\omega t) - d \sin(\omega t))$$


$$= \frac{1}{2} (ac + bd)$$

$$f^* = (a - ib) e^{-i\omega t}$$

$$g = (c + id) e^{i\omega t}$$

---


$$ac + bd$$

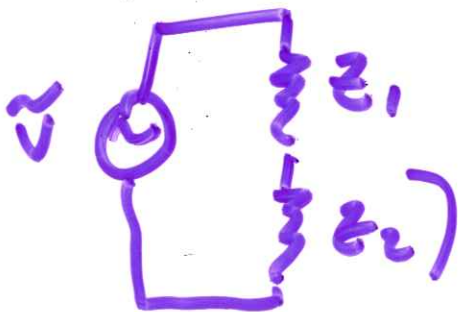


$$I = \frac{\tilde{V}}{z_1 + z_2}$$

$$V = \frac{z_2}{z_1 + z_2} \tilde{V}$$

$$\frac{1}{2} \frac{1}{(z_1 + z_2)^*} \frac{z_2}{z_1 + z_2}$$

$$I_n(z_1 + z_2) = 0$$

$$\frac{R_2}{(R_1 + R_2)^2}$$

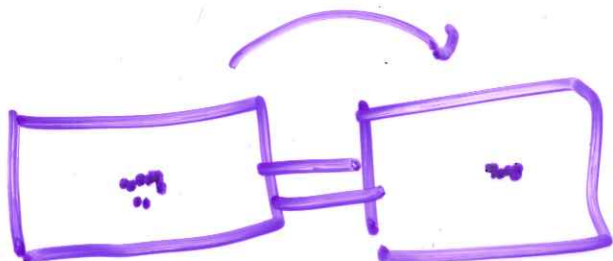

$z_i \gg z_0$

